

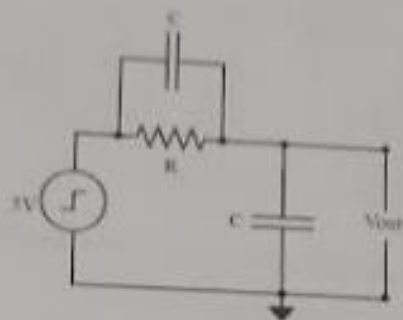


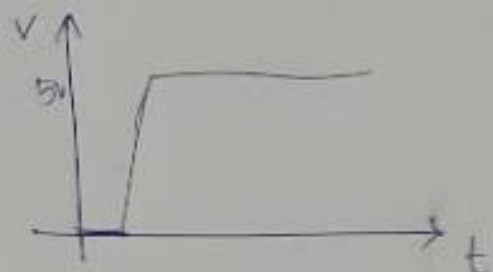7. Draw the step response of the following circuit.



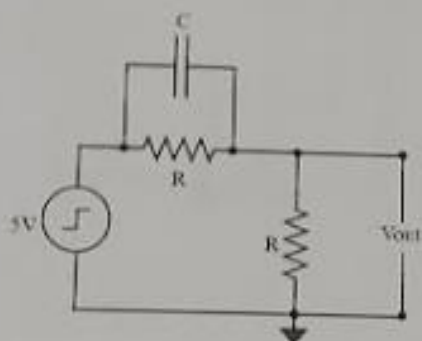8. Draw the step response of the following circuit.



9. For a long time  $C_1$  connected to point 'a' through switch 'SI'. At  $t=0+$ ,  $C_1$  connected to point 'b'. Draw the wave form at the output.

