
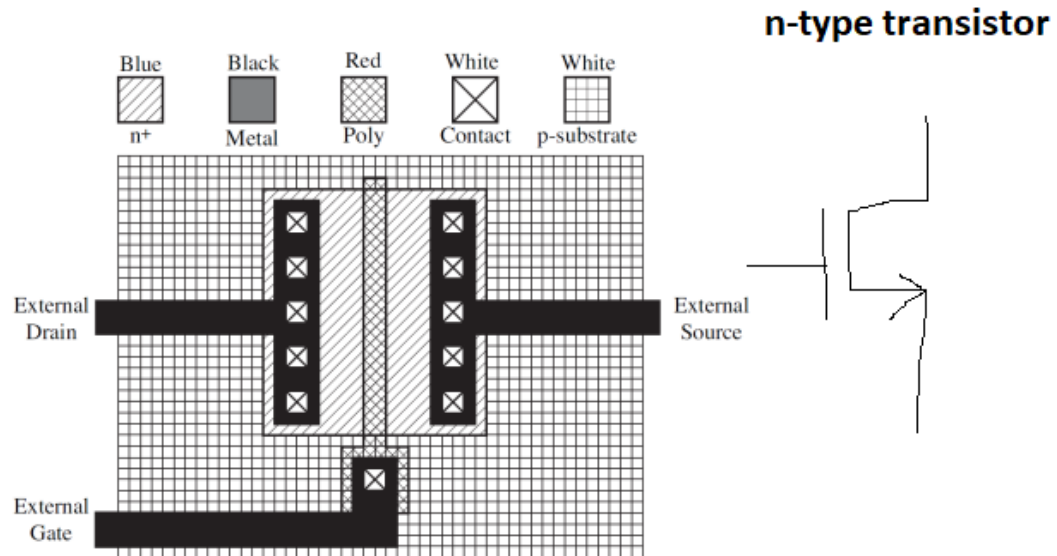


Assignment: Fabrication Process and Layout


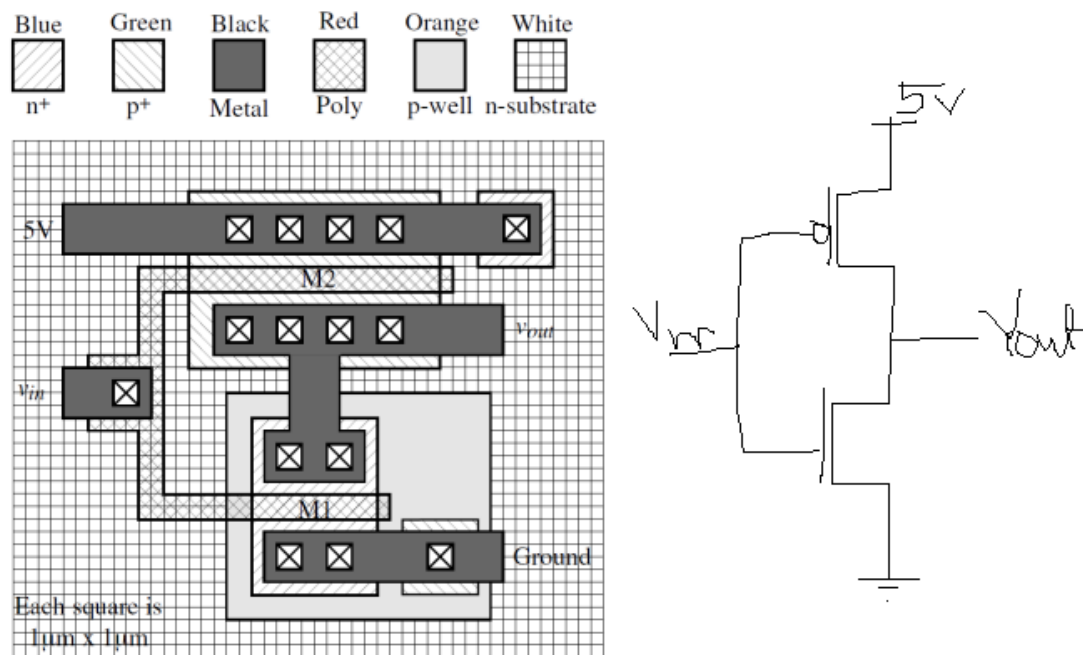
1. Draw the schematic of the below layout.




2. Draw the schematic of the below layout.



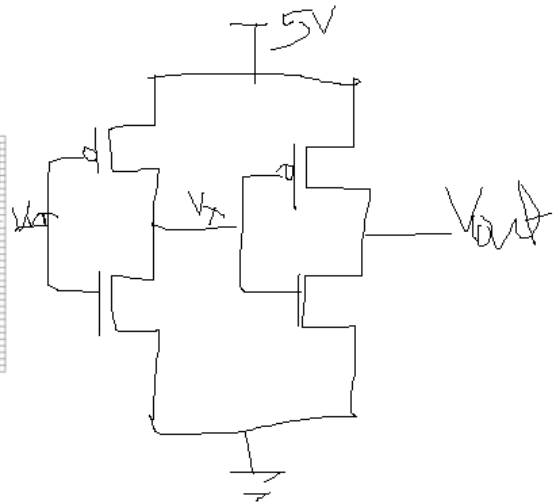
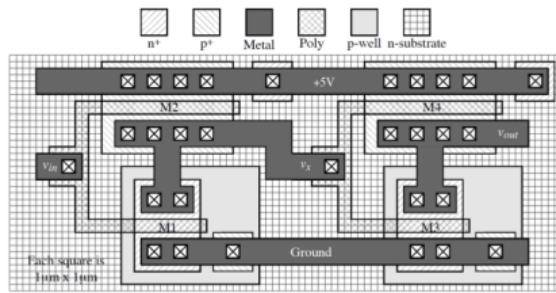
3. Draw the schematic of the below layout.



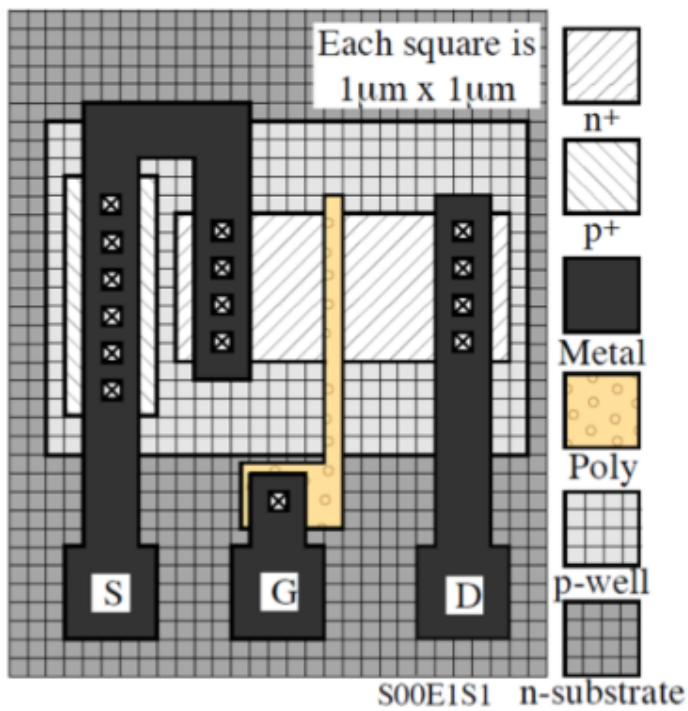4. Draw the schematic of the below layout.



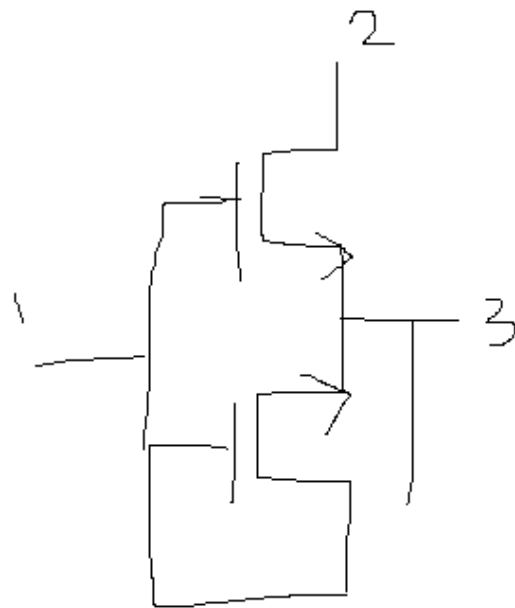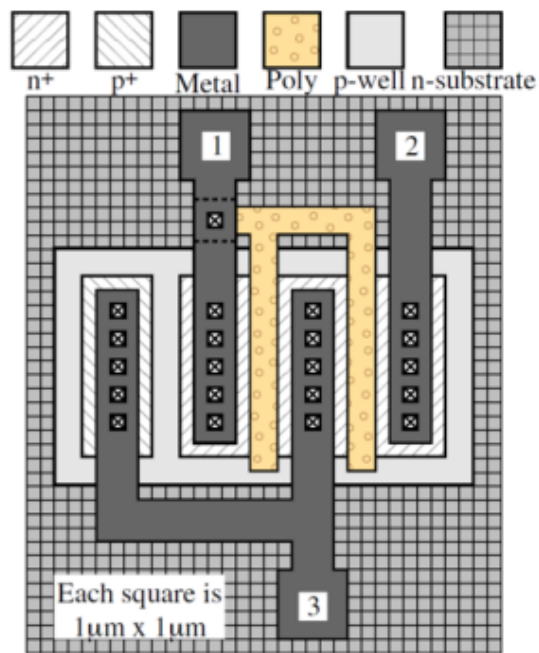5. Draw the schematic of the below layout.



6. Draw the schematic of the below layout.



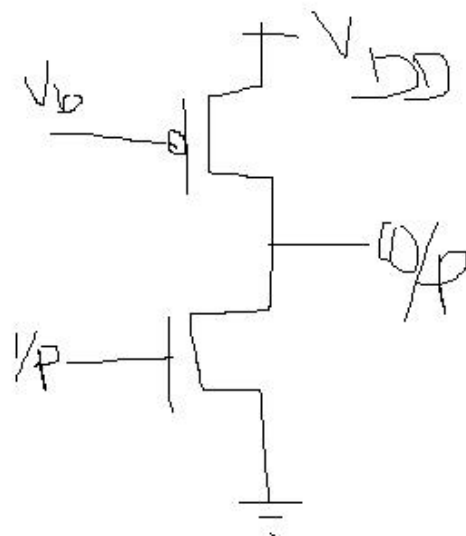
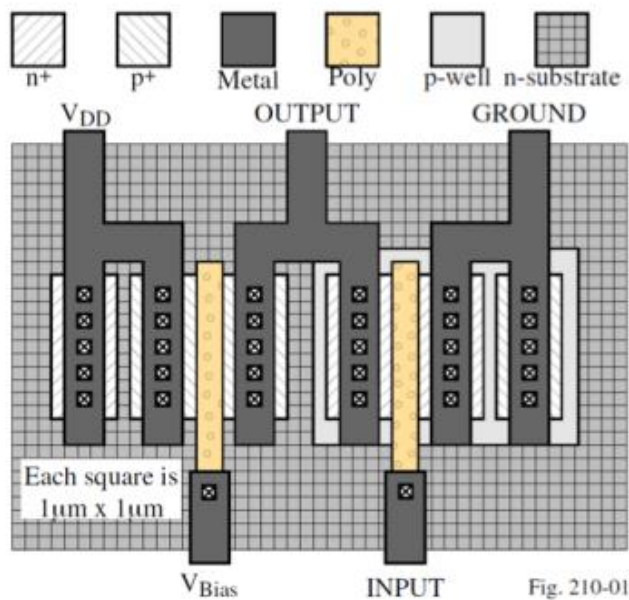


Fig. 210-01

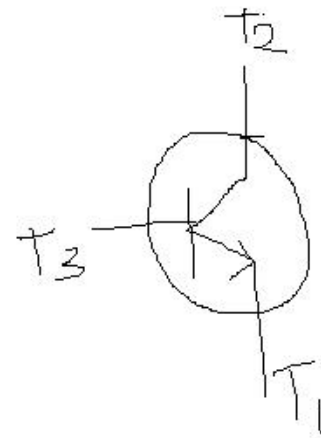7. Draw the schematic of the below layout.



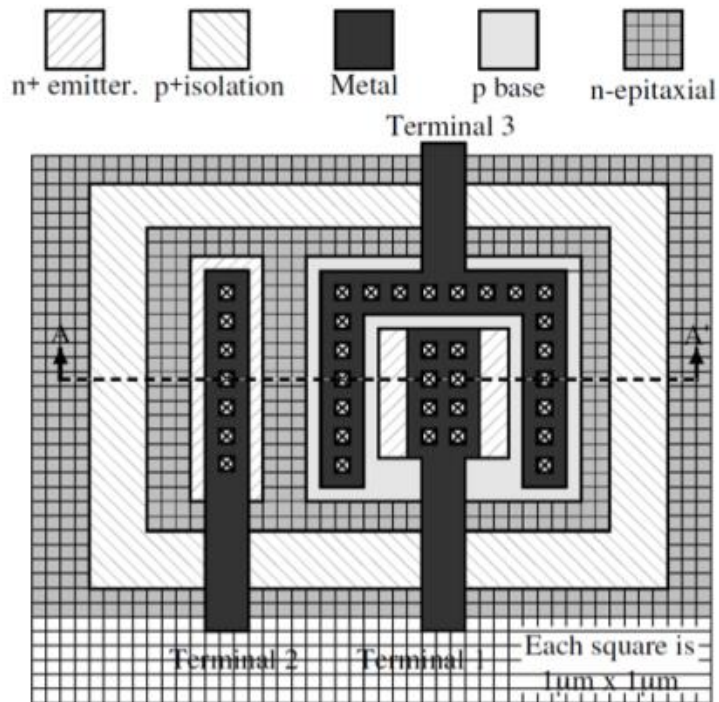8. Draw the schematic of the below layout.

